

NGSPICE :-


- Netlist \Rightarrow interconnection of elements.
- Model Files \Rightarrow Describes the physical behavior of active elements.
(.include TSMC-180nm.t, UMC 180nm, IBM 180nm etc).
nmos / pmos
- DC, AC, transient, noise etc.

How to write a Netlist?

1) Heading.

2) include files .include TSMC-180nm

3) Ckt description

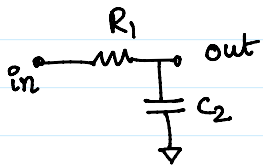

→ Capacitors

↳ C1 a b 1pF

→ Resistor

↳ R1 a b 1k Ω

→ Voltage sources.

V1 in gnd

*Sine \rightarrow sin (0 26mV 1kz 0 0 0)
 DC offset amplitude freq. delay damping factor phase

*AC \rightarrow ac 1

*pulse \rightarrow pulse (V1 V2 delay rise fall on period time period)
 highest voltage lowest voltage

highest voltage lowest voltage

M₁ Drain Gate Source Body Model W={ } L={ }
 + AS={ } PS={ } AD={ } PD={ }

Parasitic capacitances ⇒ $\left. \begin{array}{l} \text{Perimeter } C_{jsw} \\ \text{Area } C_j \end{array} \right\}$

* subckt


4) Analysis

* .dc V_{in} init. final. step.
 0 1 0.1

* .tran 0.1u 60u

* .ac dec 10 10K 10MEG
 oct " " "
 lin " " "

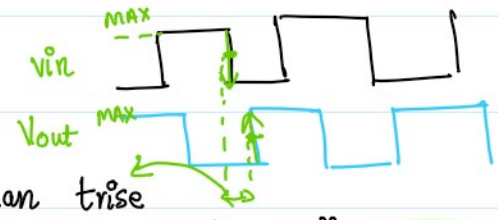.measure tran trise
 +TRIG V(in) VAL="MAX/2" FAIL=1
 +TARG V(out) VAL="MAX/2" RISE=1



5) Control commands

. control
 run
 plot V(in) V(out) - - - -
 plot dB(-V(out)/V(in))

↓
 log

.endc